



# Arithmetic Logic Unit (ALU)

Abed Al Rida Nehme 202303149

Dany Al Aawar 202301541

Hassan Fakih 202302716

# A

## Input registers

- In an Arithmetic Logic Unit (ALU), the 7474 IC (Integrated Circuit) serves as a crucial component, specifically in managing the input registers. The 7474 IC is a dual D-type flip-flop that can store data temporarily. In the context of an ALU, it plays a pivotal role in holding the input values before processing.
- Each 7474 IC can store a single bit of data, thus multiple ICs are often used in parallel to handle multi-bit data in the ALU. By using the 7474 IC for input register usage, the ALU can efficiently store and manipulate binary data, enabling arithmetic and logical operations with precision and accuracy while facilitating seamless data handling within the processing unit.

# B

## control board

- The control board of an Arithmetic Logic Unit (ALU) featuring DIP switches and push buttons serves as a user interface and a means of configuring the ALU's operations. The switches determine functions such as selecting arithmetic operations (addition, subtraction, etc.), defining logic operations (AND, OR, XOR, etc.).
- Push buttons complement this setup by providing a means to trigger or execute these configurations, initiating the ALU's computation process based on the settings established via the DIP switches, providing flexibility and control over its operations for various computational tasks.

# C

## Logic functions

- Logic operations are fundamental in ALUs as they allow the manipulation of binary data. Tasks like comparison, bitwise manipulation, conditional branching, and data transformation rely on operations like AND, OR, XOR, and shifting.
- These operations are essential for executing arithmetic calculations, handling memory operations, and various computational tasks in digital systems, forming the core functionalities of ALUs.

# D

## Adding/subtracting

- Addition and subtraction are essential functions in ALUs, enabling basic arithmetic calculations and numerical manipulations in digital systems.
- They serve as core operations for tasks like summation, comparison, and data manipulation, forming fundamental building blocks for various computational processes.



# **Project components**

# Project components

## 74LS138

A decoder that selects one of its eight outputs based on binary input, providing efficient signal decoding in digital systems and offering versatile output control in various electronic applications.

# Project components

## 74LS138

A decoder that selects one of its eight outputs based on binary input, providing efficient signal decoding in digital systems and offering versatile output control in various electronic applications.

## 74LS74

dual D-type flip-flop chip used for storing a single bit of data in digital circuits, crucial for temporary data storage in various electronic applications.

# Project components

## 74LS138

A decoder that selects one of its eight outputs based on binary input, providing efficient signal decoding in digital systems and offering versatile output control in various electronic applications.

## 74LS74

dual D-type flip-flop chip used for storing a single bit of data in digital circuits, crucial for temporary data storage in various electronic applications.

## 74LS83

4-bit binary adder chip, enabling addition operations on four-bit binary numbers in digital circuits, ideal for arithmetic calculations in various applications.

# Project components

## 74LS138

A decoder that selects one of its eight outputs based on binary input, providing efficient signal decoding in digital systems and offering versatile output control in various electronic applications.

## 74LS74

dual D-type flip-flop chip used for storing a single bit of data in digital circuits, crucial for temporary data storage in various electronic applications.

## 74LS83

4-bit binary adder chip, enabling addition operations on four-bit binary numbers in digital circuits, ideal for arithmetic calculations in various applications.

## Logic Function

AND, OR, NOT, XOR (Exclusive OR),  
NAND, NOR, XNOR (Exclusive NOR).

# Project components

## 74LS138

A decoder that selects one of its eight outputs based on binary input, providing efficient signal decoding in digital systems and offering versatile output control in various electronic applications.

## 74LS74

dual D-type flip-flop chip used for storing a single bit of data in digital circuits, crucial for temporary data storage in various electronic applications.

## 74LS83

4-bit binary adder chip, enabling addition operations on four-bit binary numbers in digital circuits, ideal for arithmetic calculations in various applications.

## Logic Function


AND, OR, NOT, XOR (Exclusive OR), NAND, NOR, XNOR (Exclusive NOR).



# Project components
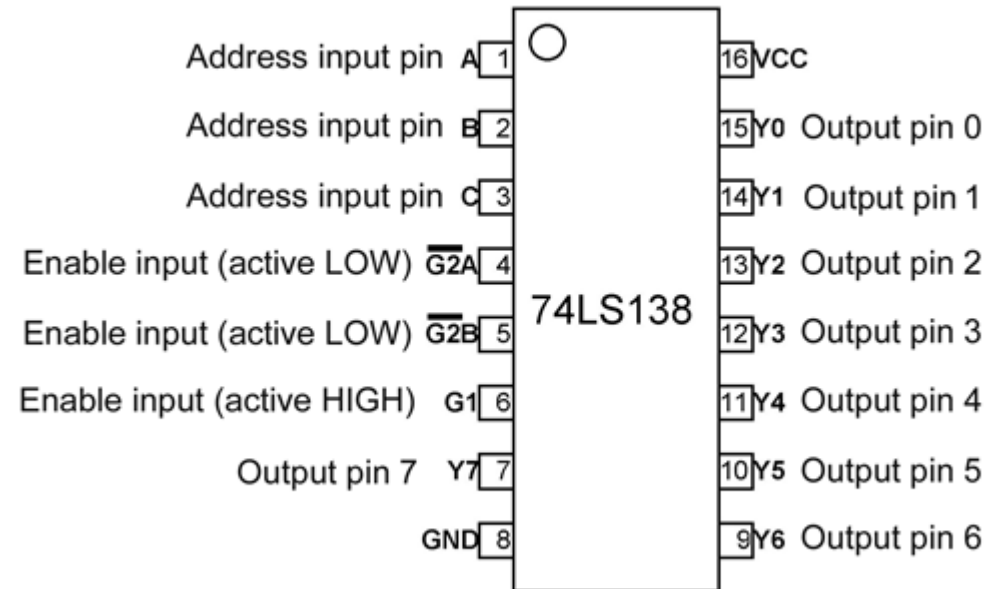
## 74LS138

A decoder that selects one of its eight outputs based on binary input, providing efficient signal decoding in digital systems and offering versatile output control in various electronic applications.



# Project components

## 74LS138

A decoder that selects one of its eight outputs based on binary input, providing efficient signal decoding in digital systems and offering versatile output control in various electronic applications.

## 74LS74

dual D-type flip-flop chip used for storing a single bit of data in digital circuits, crucial for temporary data storage in various electronic applications.

## 74LS83

4-bit binary adder chip, enabling addition operations on four-bit binary numbers in digital circuits, ideal for arithmetic calculations in various applications.


## Logic Function

AND, OR, NOT, XOR (Exclusive OR), NAND, NOR, XNOR (Exclusive NOR).

# Project components
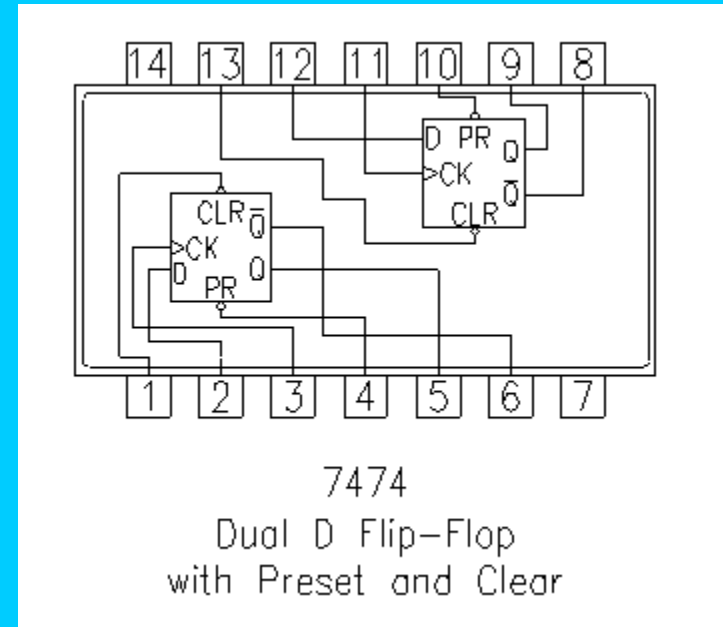
## 74LS74

dual D-type flip-flop chip used for storing a single bit of data in digital circuits, crucial for temporary data storage in various electronic applications.



# Project components

## 74LS138

A decoder that selects one of its eight outputs based on binary input, providing efficient signal decoding in digital systems and offering versatile output control in various electronic applications.

## 74LS74

dual D-type flip-flop chip used for storing a single bit of data in digital circuits, crucial for temporary data storage in various electronic applications.


## 74LS83

4-bit binary adder chip, enabling addition operations on four-bit binary numbers in digital circuits, ideal for arithmetic calculations in various applications.

## Logic Function

AND, OR, NOT, XOR (Exclusive OR), NAND, NOR, XNOR (Exclusive NOR).

# Project components

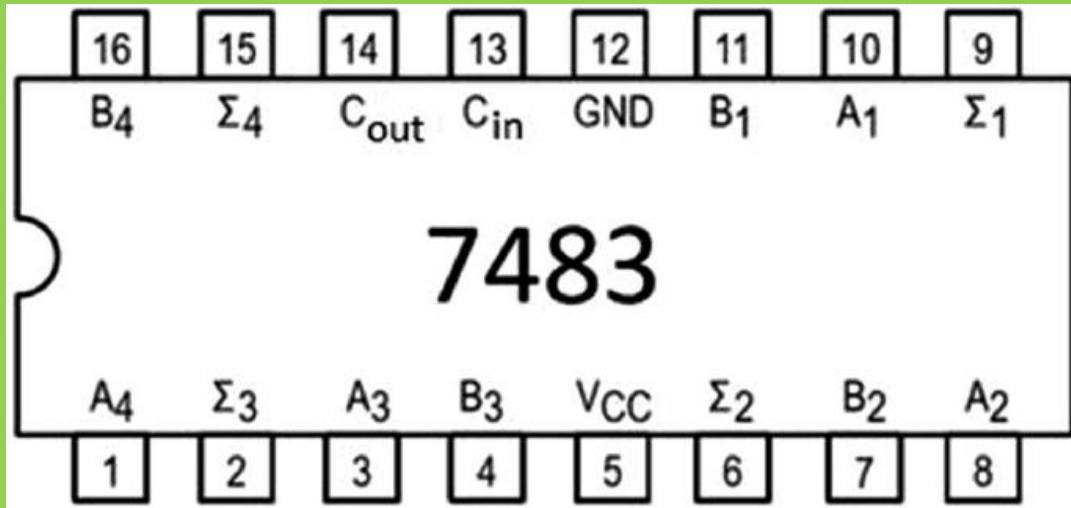

## 74LS83

4-bit binary adder chip, enabling addition operations on four-bit binary numbers in digital circuits, ideal for arithmetic calculations in various applications.

# Project components

## 74LS138

A decoder that selects one of its eight outputs based on binary input, providing efficient signal decoding in digital systems and offering versatile output control in various electronic applications.

## 74LS74

dual D-type flip-flop chip used for storing a single bit of data in digital circuits, crucial for temporary data storage in various electronic applications.


## 74LS83

4-bit binary adder chip, enabling addition operations on four-bit binary numbers in digital circuits, ideal for arithmetic calculations in various applications.

## Logic Function

AND, OR, NOT, XOR (Exclusive OR), NAND, NOR, XNOR (Exclusive NOR).

# Project components

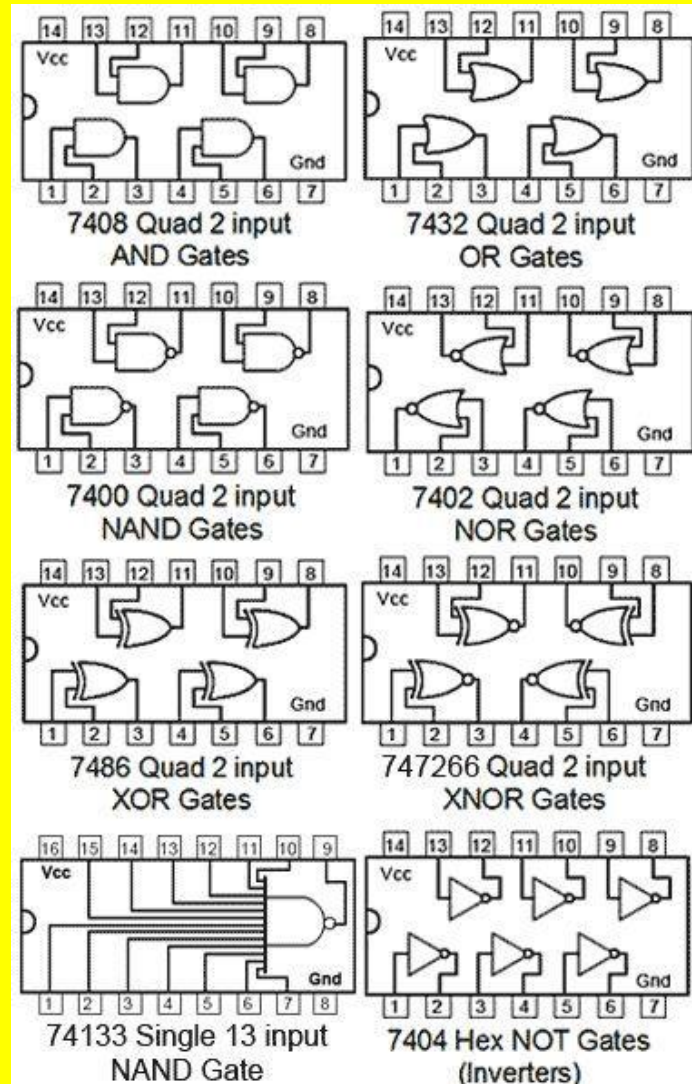

## Logic Function

AND, OR, NOT, XOR (Exclusive OR),  
NAND, NOR, XNOR (Exclusive NOR).

# Project components

## 74LS138

A decoder that selects one of its eight outputs based on binary input, providing efficient signal decoding in digital systems and offering versatile output control in various electronic applications.

## 74LS74

dual D-type flip-flop chip used for storing a single bit of data in digital circuits, crucial for temporary data storage in various electronic applications.

## 74LS83

4-bit binary adder chip, enabling addition operations on four-bit binary numbers in digital circuits, ideal for arithmetic calculations in various applications.

## Logic Function

AND, OR, NOT, XOR (Exclusive OR), NAND, NOR, XNOR (Exclusive NOR).



# Future work

1-an 8 bit ALU

2-controlling it using a keypad

3-displaying the results

# Future work

## 1-an 8 bit ALU

2-controlling it using a keypad

3-displaying the results

- To transform a 4-bit register into an 8-bit register, you need to add four more bits to the existing register. This can be achieved by concatenating four additional bits to the original 4-bit data.
- That means we need to use 4 more 7474 chips for the register as well as on more 7483 and double the number of the logic gates.
- We need to Connect the C-out (carry-out) of the first 7483 to the C-in (carry-in) of the second 7483.

# Future work

1-working on expanding it to an 8 bit ALU

2-controlling it using a keypad

3-displaying the results

# Future work

1-an 8 bit ALU

**2-controlling it using a keypad**

3-displaying the results

- Connect the rows and columns of the keypad to the appropriate pins on the 74C922 IC.
- This step enhance the program even more due to it being easier to use by the user.

# Future work

1-working on expanding it to an 8 bit ALU

2-controlling it using a keypad

3-displaying the results

# Future work

1-an 8 bit ALU

2-controlling it using a keypad

**3-displaying the results**

- Connect the outputs of your decoder (which represent the binary-coded decimal or other code for each digit) to the inputs of the seven-segment display.
- If you have multiple seven-segment displays to show multi-digit numbers, you might need to implement multiplexing. In this case, rapidly cycle through the displays and update the segments for each digit.

# Future work

1-working on expanding it to an 8 bit ALU

2-controlling it using a keypad

3-displaying the results

Thank you!!!